
Adan Partida, Jr.

Professor Olin Hartin

EEE333

Lab 2

#### **ALU Test Bench Waveform:**

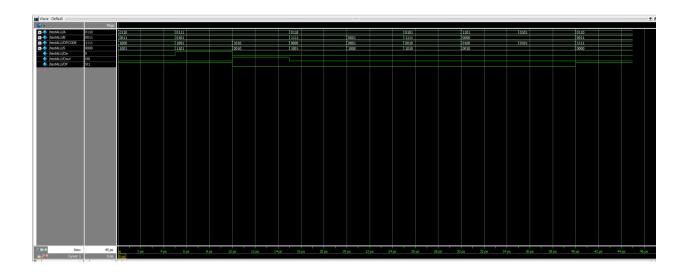


### **ALU Test Bench Table:**


**Test Bench Tests** 

#	Operation	aluin_a	aluin_b	Cin	alu_out	Cout	OF				
1	add	0110	0011	0	1001	0					
2	add with Cin	0111	0101	1	101	0	ĺ				
3	sub b from a	0111	0101	0	0010	1	0				
4	Bitwise NAND	0110	1111	0	1001	0	9				
5	Bitwise NOR	0110	0001	0	1000	Q	O				
6	Bitwise XOR	0101	1111	0	1610	9	Q				
7	Bitwise NOT	1101	0000	0	0010	O					
8	logical right shift	0101	0000	0	0010	Q	0				
result											
						Carry					
		aluin_a	aluin_b	Cin	Result	out	Overflow				
9	Function given	0110	0011	0	0000	0	l				

### **ALU Board Programming:**

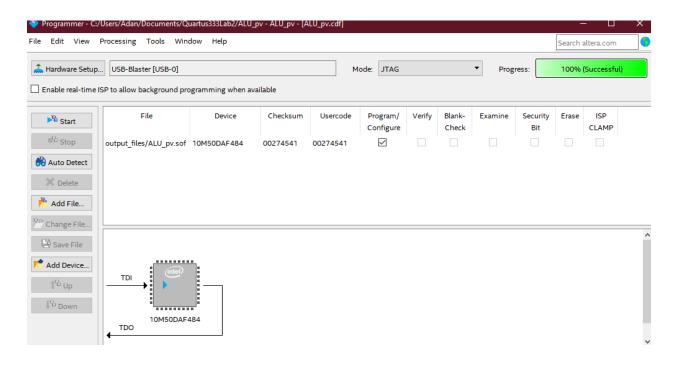

#### **Pin Assignments:**

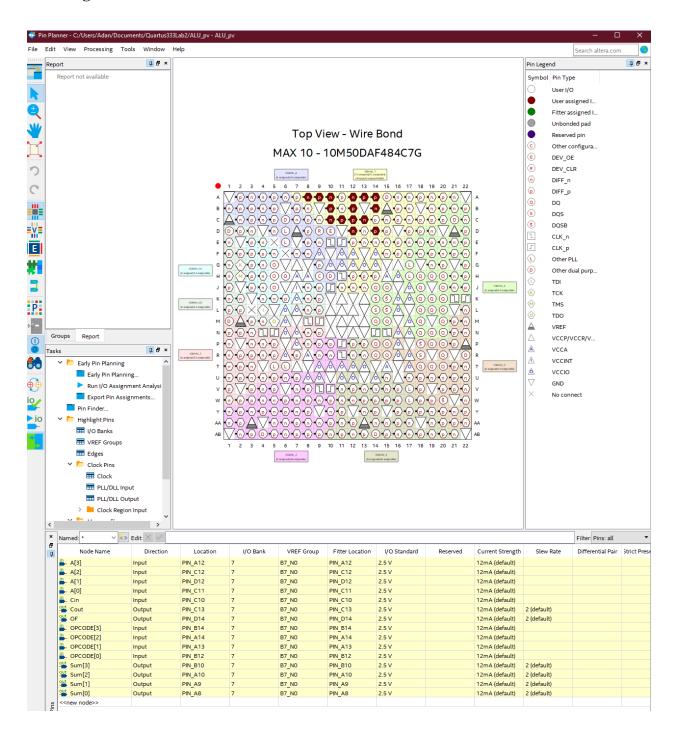


# **Physical Board Pics:**


## #1 add:



### #2 add with Cin:

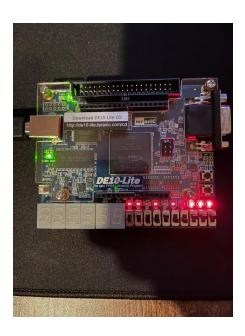

### #3 sub b from a:

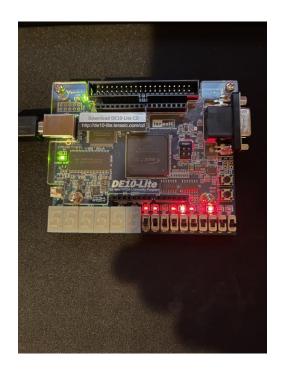

**#4 Bitwise NAND:** 




### **#5 Bitwise NOR:**




### #6 Bitwise XOR:



### **#7 Bitwise NOT:**

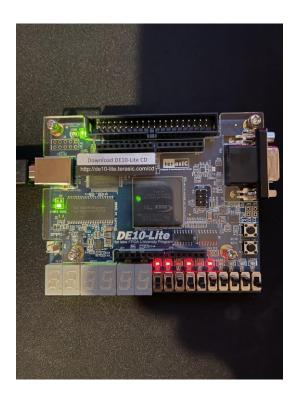

## #8 logical right shift:

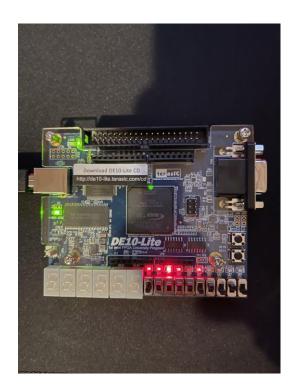

#### **ALU Physical Board Demo Table:**

#### **Demo**

Take a snapshot showing the window that indicates your board is programmed (the progress bar should show 100% and include the full programming window in the image. And paste it into power point along with an image showing your pin assignments. Label each image and make sure it is clear.

#	Operation	aluin_a	aluin_b	Cin	alu_out	Cout	OF			
1	add	0011	0011	0	Ollo	0	O			
2	add with Cin	0011	0011	1	oll	0	0			
3	sub b from a	0111	0011	0	0100	0				
4	Bitwise NAND	0110	0011	0	1101	ð	0			
5	Bitwise NOR	0110	0011	0	1000	O	O			
6	Bitwise XOR	0101	0011	0	0110	0	0			
7	Bitwise NOT	1111	0011	0	0000	0	0			
8	logical right shift	0101	0011	0	0000	0	1			
note, hardcoded										